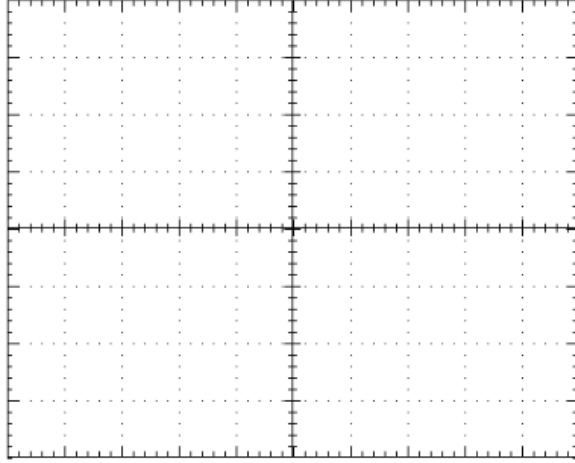


EXPERIMENT RESULTS

1. Single Phase Full-Wave Uncontrolled Rectifier




$V_{i(max)}$:

$V_{i(rms)}$:

$V_{o(ort)}$:

$V_{o(rms)}$:

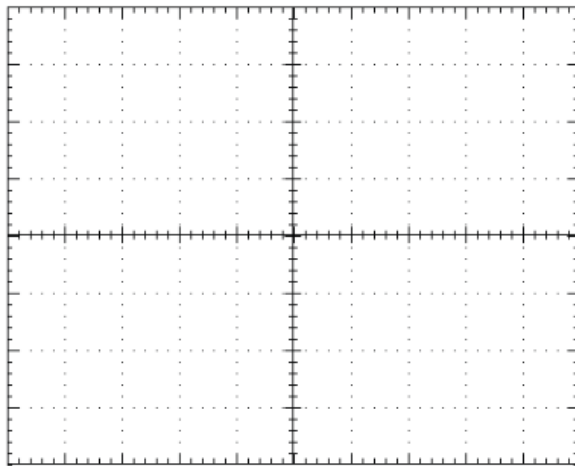(a) Input and Output Voltage (Ohmic Load)




$V_{o(ort)}$:

$V_{o(rms)}$:

$I_{o(ort)}$:


$I_{o(rms)}$:

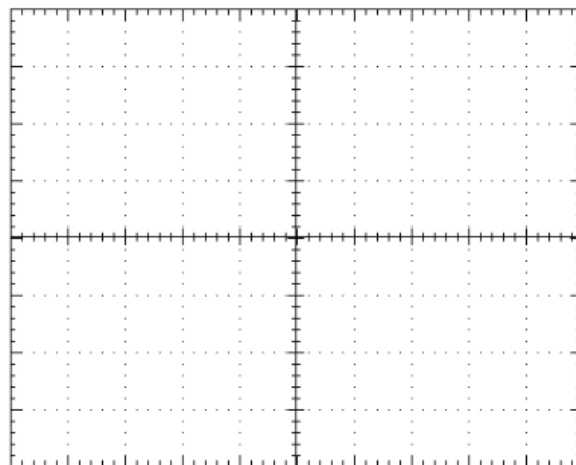(b) Output Voltage and Current (Ohmic Load)



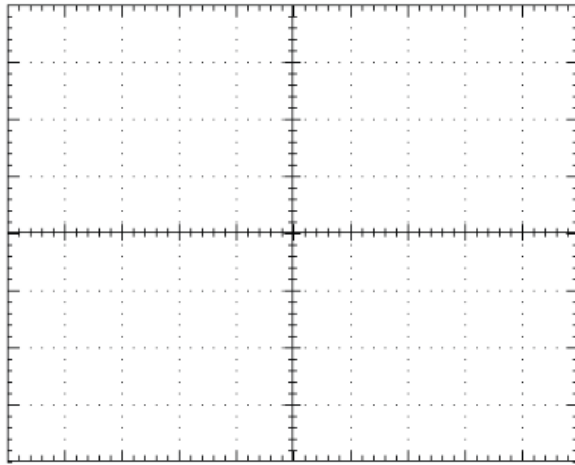(c) D1 and D2 Diode Voltages (Ohmic Load)

Single Phase Full-Wave Uncontrolled and Controlled Rectifier



$V_{o(ort)}$:

$V_{o(rms)}$:

$I_{o(ort)}$:

$I_{o(rms)}$:

(d) Output Voltage and Current (Inductive Load)

- Using the measurements taken for the ohmic load, calculate the following rectifier power.


$$P_{o(ort)} = \frac{V_{o(ort)}^2}{R} = V_{o(ort)} I_{o(ort)} \quad :$$

$$P_{o(rms)} = \frac{V_{o(rms)}^2}{R} = V_{o(rms)} I_{o(rms)} \quad :$$

- Discuss the obtained results.

Single Phase Full-Wave Uncontrolled and Controlled Rectifier

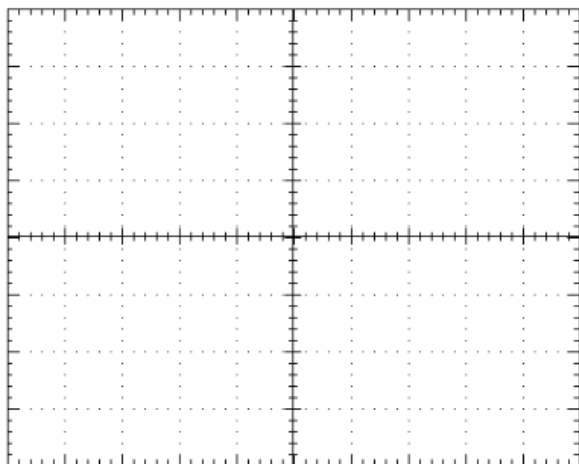
2. Single Phase Full Wave Controlled Rectifier



$$\alpha = 30^\circ$$

$V_{o(ort)}$:

$V_{o(rms)}$:

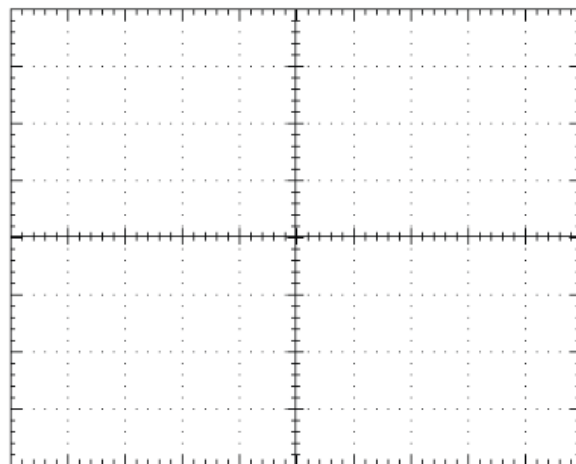


$$\alpha = 60^\circ$$

$V_{o(ort)}$:

$V_{o(rms)}$:

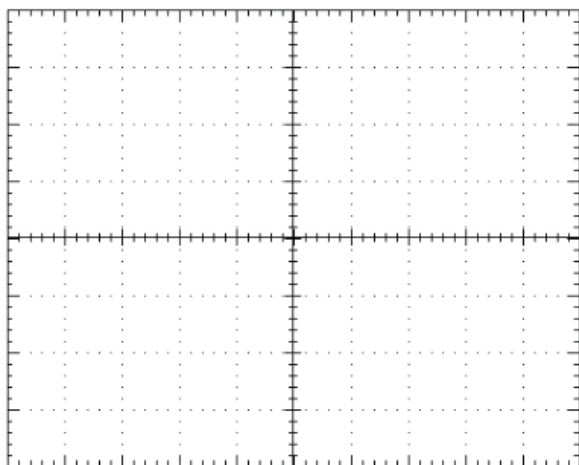
(a) Input and Output Voltage (Ohmic Load)



$$\alpha = 30^\circ$$

$I_{o(ort)}$:

$I_{o(rms)}$:

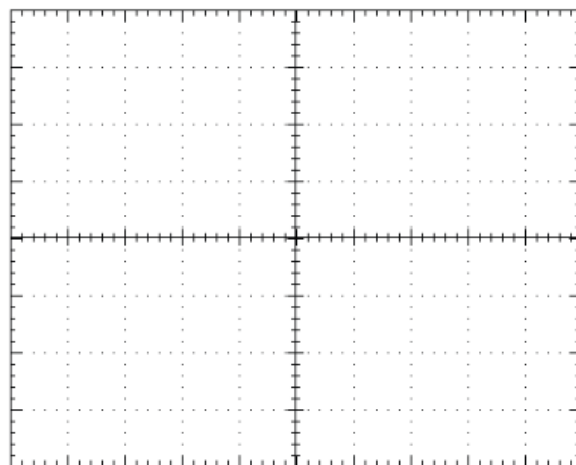


$$\alpha = 60^\circ$$

$I_{o(ort)}$:


$I_{o(rms)}$:

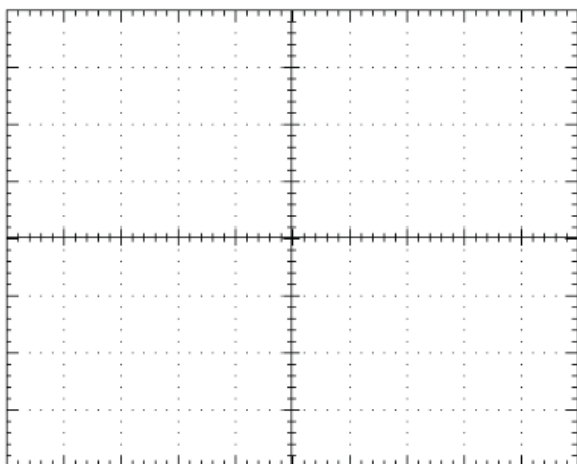(b) Output Voltage and Current (Ohmic Load)

Single Phase Full-Wave Uncontrolled and Controlled Rectifier




$\alpha = 30^\circ$

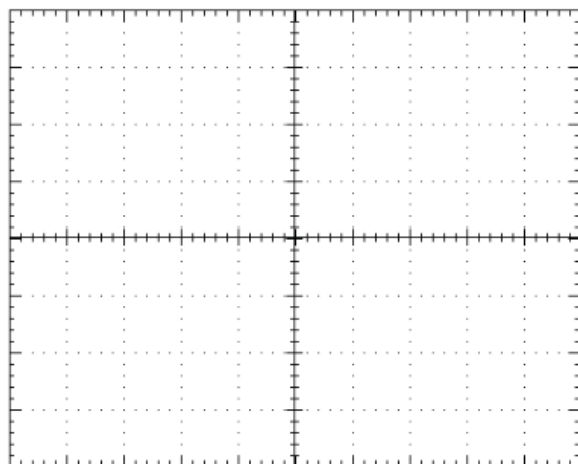


$\alpha = 60^\circ$

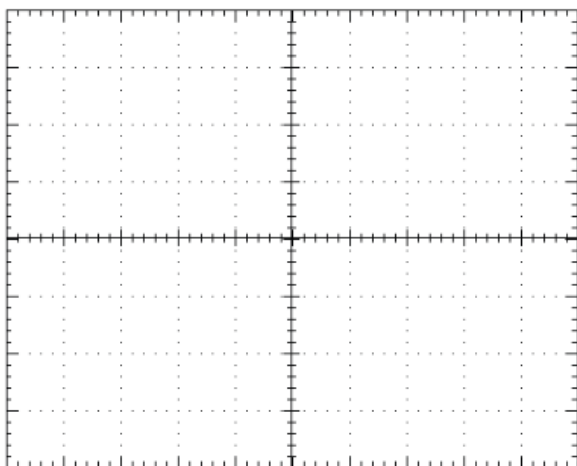(c) T1 and T2 Thyristor Voltage (Ohmic Load)



$\alpha = 30^\circ$

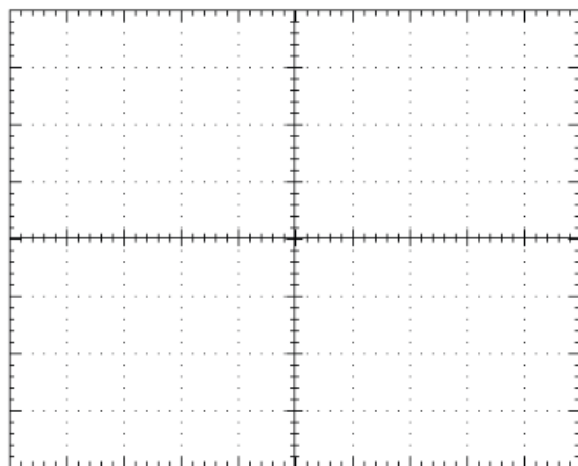

$\alpha = 60^\circ$

$V_{o(ort)}$

:

$V_{o(ort)}$

:

$V_{o(rms)}$

:

$V_{o(rms)}$

:

$I_{o(ort)}$

:

$I_{o(ort)}$

:

$I_{o(rms)}$

:

$I_{o(rms)}$

:

(d) Output Voltage and Current (Inductive Load)

- Discuss the obtained results.